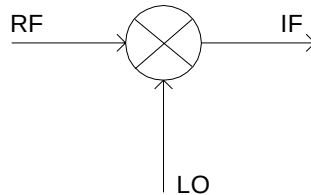


## Lecture 27: Mixers. Gilbert Cell

Mixers shift the frequency spectrum of an input signal. This is an essential component in electrical communications (wireless or otherwise) if we wish to use RF signals to convey audio or data signals over long distances, for example.

The circuit symbol for a mixer has three ports (Fig. 12.1):



Notice that all three ports have signals at **different frequencies!**

“Mixing” has a couple of **connotations**. One is that of combining (by summing) signals from different channels (or sources), as in the recording industry. Fig. 15.1 from the *ARRL Handbook* on the next page illustrates this principle.

Clearly, this is not the type of “mixing” that’s needed in communications. We need to **shift** the frequency. This type of mixing is the result of **multiplying** signals in the time domain, as shown in Fig. 15.2 of the *ARRL Handbook*.

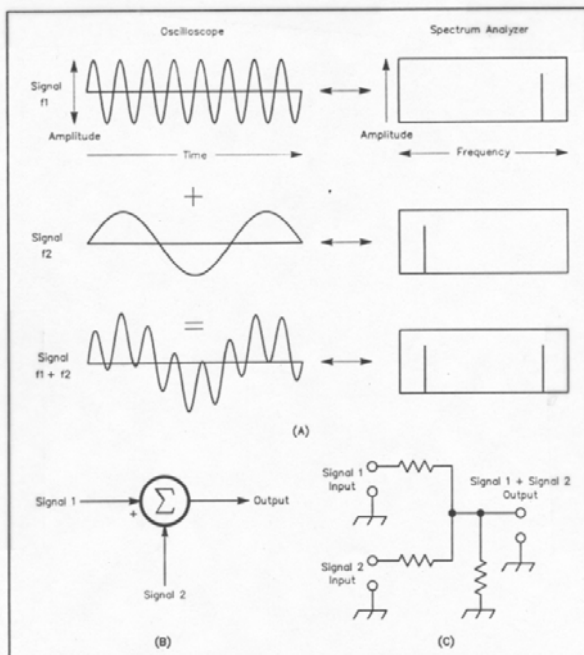


Fig 15.1—Adding or summing two sine waves of different frequencies ( $f_1$  and  $f_2$ ) combines their amplitudes without affecting their frequencies. Viewed with an oscilloscope (a real-time graph of amplitude versus time), adding two signals appears as a simple superimposition of one signal on the other. Viewed with a spectrum analyzer (a real-time graph of signal amplitude versus frequency), adding two signals just sums their spectra. The signals merely coexist on a single cable or wire. All frequencies that go into the adder come out of the adder, and no new signals are generated.

Drawing B, a block diagram of a summing circuit, emphasizes the stage's mathematical operation rather than showing circuit components. Drawing C shows a simple summing circuit, such as might be used to combine signals from two microphones. In audio work, a circuit like this is often called a mixer—but it does not perform the same function as an RF mixer.

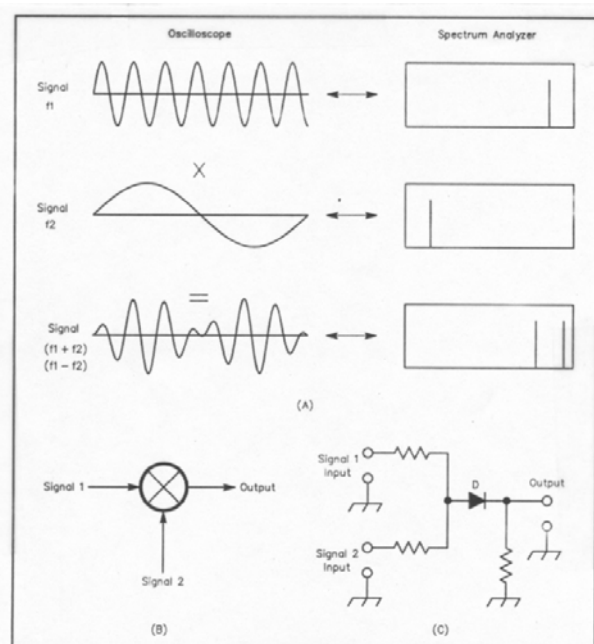


Fig 15.2—Multiplying two sine waves of different frequencies produces a new output spectrum. Viewed with an oscilloscope, the result of multiplying two signals is a composite wave that seems to have little in common with its components. A spectrum-analyzer view of the same wave reveals why: The original signals disappear entirely and are replaced by two new signals—at the sum and difference of the original signals' frequencies. Drawing B diagrams a multiplier, known in radio work as a mixer. The X emphasizes the stage's mathematical operation. (The circled X is only one of several symbols you may see used to represent mixers in block diagrams, as Fig 15.3 explains.)

Drawing C shows a very simple multiplier circuit. The diode, D, does the mixing. Because this circuit does other mathematical functions and adds them to the sum and difference products, its output is more complex than  $f_1 + f_2$  and  $f_1 - f_2$ , but these can be extracted from the output by filtering.

There are two general types of mixing circuits, those involving:


1. **Nonlinear** components, such as diodes, etc.
2. **Linear**, but **time-varying circuits**. These circuits can shift the frequency spectrum of a signal, in contrast to linear and time **in**variant circuits (which cannot).

## Gilbert Cell

All mixers in the NorCal 40A are based on the **Gilbert cell**. The Gilbert cell uses a **linear, time-varying circuit** to achieve time-domain multiplication, and hence, frequency shifting.

A Gilbert cell is shown in Fig. 12.2. The RF signal is input to a long-tailed differential amplifier, which we studied in Sec. 9.8. The collectors of Q1 and Q2 have a cross connected set of four transistors, which are driven by a local oscillator (LO).

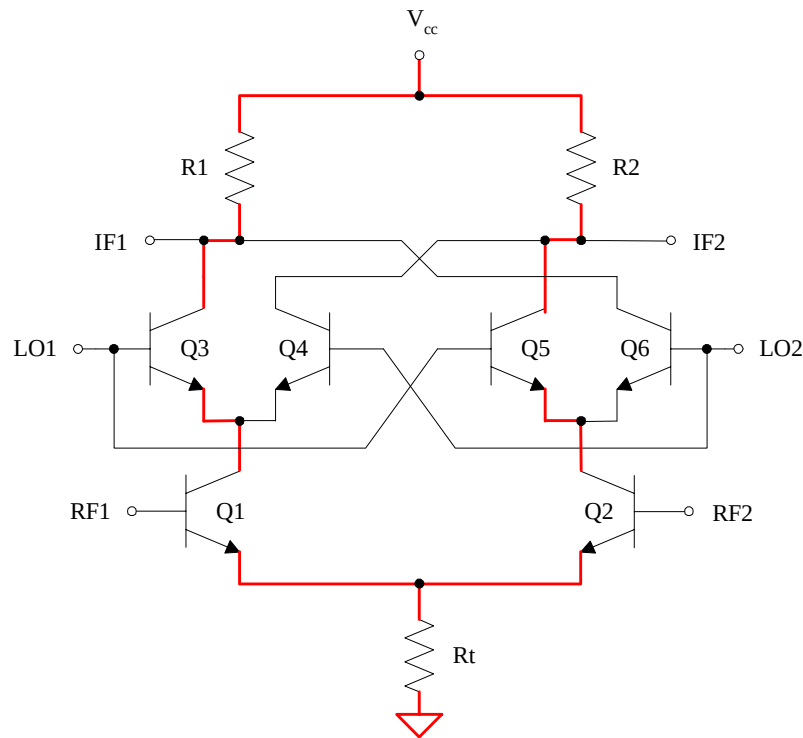To see how the Gilbert cell operates, **first** consider what happens when the voltage  $V_{LO1}$  is large enough so that Q3 and Q5 turn on and  $V_{LO2}$  is small enough, that Q4 and Q6 turn off:




Here we see that Q3 and Q5 act as closed switches so that:

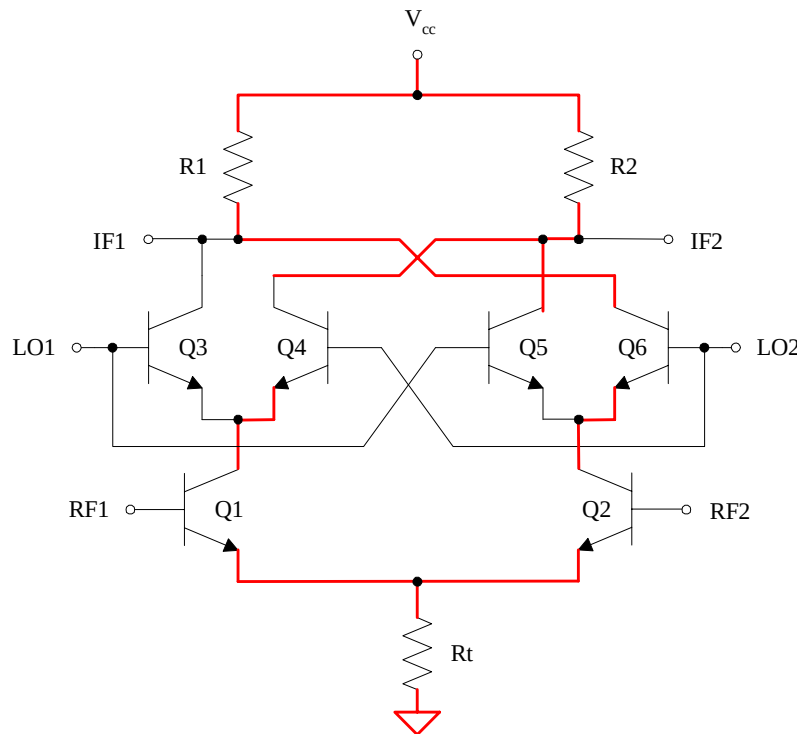- Q1 is connected to R1, and
- Q2 is connected to R2

as in a “typical” differential amplifier configuration with the output taken at, what we will call here, the “IF” terminals.

**Second**, consider what happens when the opposite input occurs. Specifically, suppose  $V_{LO2}$  is large enough so that Q4 and Q6 are on while  $V_{LO1}$  is small enough that Q3 and Q5 are off:



Now we see that Q4 and Q6 act as closed switches so that

- Q1 is connected to R2, and
- Q2 is connected to R1.

This also is a differential amplifier configuration, but with the outputs interchanged wrt to the previous case. In other words, the output (the IF) is almost the same as before. It has just been multiplied by the factor  $-1$ .

The overall function of the Gilbert cell is to multiply in the *time domain* the input RF signal (at the RF frequency) by a square wave with value  $+1$  or  $-1$  at the LO frequency! This is mixing.

The **Gilbert cell is also an active mixer** in that the IF output signal is amplified because of the differential amplifier gain. (Active mixers are very nice in the sense that they accomplish two jobs at once: they mix and they amplify.)

A Gilbert cell is the active mixer inside the **SA602AN** IC used in the NorCal 40A (see the datasheet on p. 415). As we've already seen, this IC also has part of an oscillator circuit built inside. What a versatile IC!

From Fig. 4 of the SA602AN datasheet we can see that certain subsystems are internally biased. Consequently, we don't need to construct an external bias circuit. However, **we must capacitively couple** to the SA602AN so we don't disturb this biasing (examples of this are C4, C5, C13, C15, C31 and C33).

---


## Mixer Mathematics

It is helpful to study the mathematic basis behind the Gilbert cell. This will help us understand this circuit better, as well as develop an appreciation of the mixing process in general.

Let's define the RF input voltage as

$$V_{rf}(t) = V_{rf} \cos(\omega_{rf} t) \quad (12.2)$$

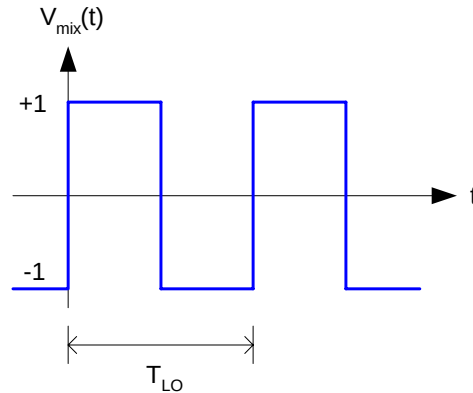and define the mixing signal (which is **not** the LO signal, as is stated in the text) by the square wave:



Since this mixing signal is a periodic waveform, we can expand it in this [Fourier series](#)

$$V_{mix}(t) = \frac{4}{\pi} \left[ \cos(\omega_{lo}t) - \frac{\cos(3\omega_{lo}t)}{3} + \frac{\cos(5\omega_{lo}t)}{5} - \dots \right] \quad (12.3)$$

as derived in Sec. 2 of Appendix B.

The Gilbert cell effectively **multiplies** both of these signals (12.2) and (12.3) **in the time domain** as

$$V(t) = V_{rf}(t) \cdot V_{mix}(t) \quad (12.4)$$

giving

$$V(t) = \frac{2V_{rf}}{\pi} \left[ \cos(\omega_{-}t) - \frac{1}{3}\cos(\omega_{3-}t) + \frac{1}{5}\cos(\omega_{5-}t) - \dots \right] + \frac{2V_{rf}}{\pi} \left[ \cos(\omega_{+}t) - \frac{1}{3}\cos(\omega_{3+}t) + \frac{1}{5}\cos(\omega_{5+}t) - \dots \right] \quad (12.5)$$

where

$$\omega_{+} = \omega_{lo} + \omega_{rf} \qquad \omega_{-} = \left| \omega_{lo} - \omega_{rf} \right|$$

$$\begin{array}{ll}
 \omega_{3+} = 3\omega_{lo} + \omega_{rf} & \omega_{3-} = |3\omega_{lo} - \omega_{rf}| \\
 \omega_{5+} = 5\omega_{lo} + \omega_{rf} & \omega_{5-} = |5\omega_{lo} - \omega_{rf}| \\
 \vdots & \vdots
 \end{array}$$

Note in (12.5) that we have the **sum and difference signals** present in the output (IF) voltage signal:

$$V_+(t) = \frac{2V_{rf}}{\pi} \cos(\omega_+ t) \quad (12.6)$$

and 
$$V_-(t) = \frac{2V_{rf}}{\pi} \cos(\omega_- t) \quad (12.7)$$

as well as the **third-harmonic** terms:

$$V_{3+}(t) = -\frac{2V_{rf}}{3\pi} \cos(\omega_{3+} t) \quad (12.10)$$

and 
$$V_{3-}(t) = -\frac{2V_{rf}}{3\pi} \cos(\omega_{3-} t) \quad (12.11)$$

and the **fifth-harmonic** terms:

$$V_{5+}(t) = \frac{2V_{rf}}{5\pi} \cos(\omega_{5+} t)$$

and 
$$V_{5-}(t) = \frac{2V_{rf}}{5\pi} \cos(\omega_{5-} t)$$

and all **higher-ordered odd harmonics**.

Observe that the amplitudes of these harmonics are decreasing with increasing harmonic number.

Also note that the RF signal, the LO signal and the **even** mixer **harmonics** are **not present** in the output. Nice! This occurs because the Gilbert cell is a **balanced mixer**. However, in reality some (or all) of these signal components will be present in the output since we won't have a perfectly balanced mixer.

---

## NorCal 40A Mixers

There are three mixers in the NorCal 40A. You'll install the:

1. **RF Mixer** in Prob. 28,
2. **Product Detector** in Prob. 29, and
3. **Transmit Mixer** in Prob. 30.

In addition, using the measured spectrum from the output of the Transmit Mixer shown in Fig. 12.15, you will identify the various harmonics using

$$f_{mn} = mf_{vfo} \pm nf_{to} \quad (12.46)$$

There is a misprint of this equation in the text.

---

## Conversion Gain

Gain (or loss) of a mixer is characterized with a power gain expression similar to any amplifier



$$G = \frac{P}{P_+} \quad (12.1)$$

where  $G$  is called the **conversion gain**,  $P$  is the output IF power and  $P_+$  is the available power from the RF source.

Here, however, the input and output frequencies of the two signals are different.